

# **NODE ANALYSIS**

# Circuit terminologies: (Branch, Node)

- **Branch:** It represents single circuit element such as voltage source, resistor, etc.
- **Node:** A point in a network where two or more elements are connected is called node.

# NODAL ANALYSIS

**Nodal analysis**—a method that provides the nodal voltages of a network, that is, the voltage from the various **nodes**(junction points) of the network to ground.

*The number of nodes for which the voltage must be determined using nodal analysis is 1 less than the total number of nodes.*

*The number of equations required to solve for all the nodal voltages of a network is 1 less than the total number of independent nodes.*


# NODAL ANALYSIS

## Nodal Analysis Procedure

- 1. Determine the number of nodes within the network.*
- 2. Pick a reference node, and label each remaining node with a subscripted value of voltage:  $V_1$ ,  $V_2$ , and so on.*
- 3. Apply Kirchhoff's current law at each node except the reference.*
- 4. Solve the resulting equations for the nodal voltages.*

# NODAL ANALYSIS

**EXAMPLE 8.19** Apply nodal analysis to the network in Fig. 8.46

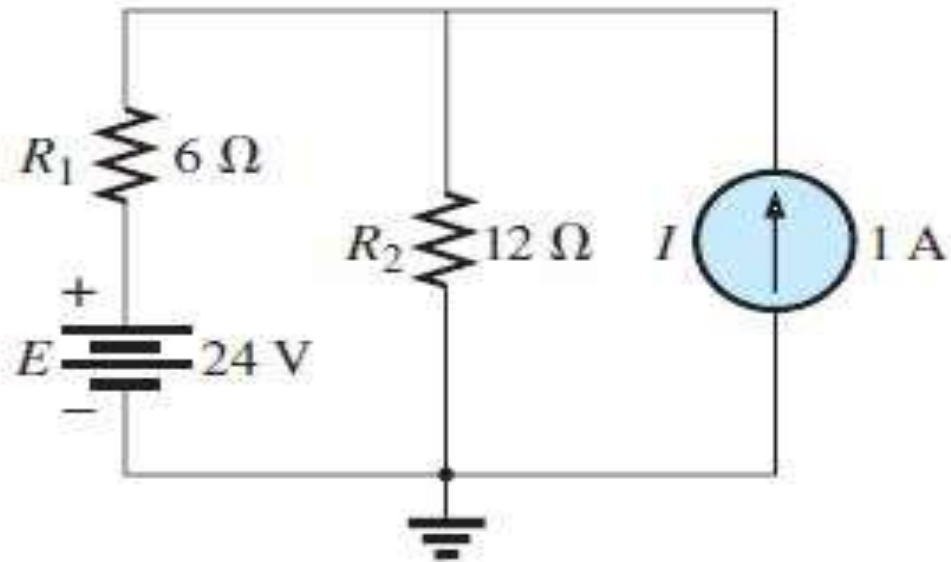


**FIG. 8.46**

*Example 8.19.*

# NODAL ANALYSIS

## ***Solution:***

*Steps 1 and 2:* The network has two nodes, as shown in Fig. 8.47. The lower node is defined as the reference node at ground potential (zero volts), and the other node as  $V_1$ , the voltage from node 1 to ground.

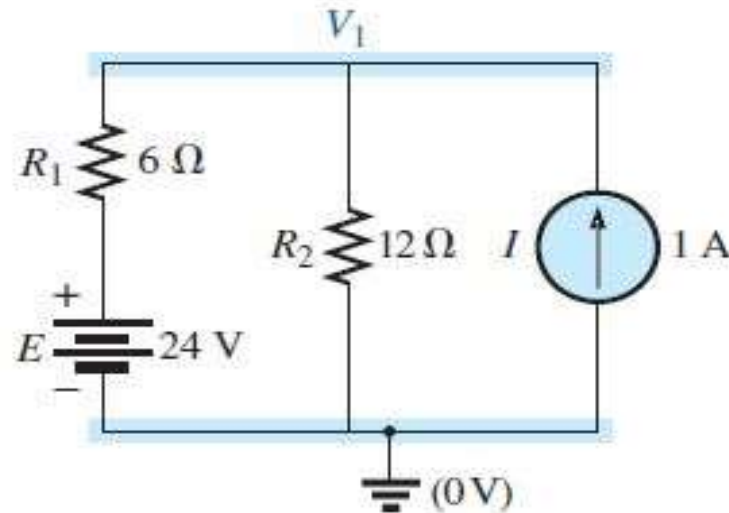

**FIG. 8.47**

*Network in Fig. 8.46 with assigned nodes.*

# NODAL ANALYSIS


## ***Solution:***

*Step 3:*  $I_1$  and  $I_2$  are defined as leaving the node in Fig. 8.48, and Kirchhoff's current law is applied as follows:

$$I = I_1 + I_2$$

The current  $I_2$  is related to the nodal voltage  $V_1$  by Ohm's law:

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{V_1}{R_2}$$

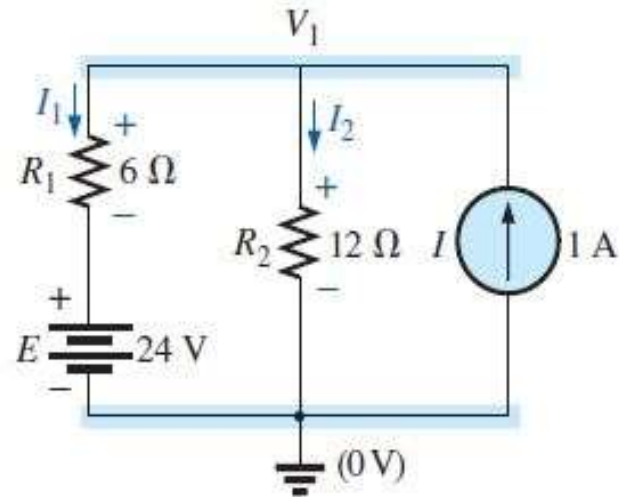

**FIG. 8.48**

*Applying Kirchhoff's current law to the node  $V_1$ .*

# NODAL ANALYSIS

The current  $I_1$  is also determined by Ohm's law as follows:

$$I_1 = \frac{V_{R_1}}{R_1}$$

with

$$V_{R_1} = V_1 - E$$

Substituting into the Kirchhoff's current law equation:

$$I = \frac{V_1 - E}{R_1} + \frac{V_1}{R_2}$$

and rearranging, we have

$$I = \frac{V_1}{R_1} - \frac{E}{R_1} + \frac{V_1}{R_2} = V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{E}{R_1}$$

or

$$V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{E}{R_1} + 1$$

Substituting numerical values, we obtain


$$V_1 \left( \frac{1}{6 \Omega} + \frac{1}{12 \Omega} \right) = \frac{24 \text{ V}}{6 \Omega} + 1 \text{ A} = 4 \text{ A} + 1 \text{ A}$$

$$V_1 \left( \frac{1}{4 \Omega} \right) = 5 \text{ A}$$

$$V_1 = 20 \text{ V}$$

The currents  $I_1$  and  $I_2$  can then be determined using the preceding equations:

$$\begin{aligned} I_1 &= \frac{V_1 - E}{R_1} = \frac{20 \text{ V} - 24 \text{ V}}{6 \Omega} = \frac{-4 \text{ V}}{6 \Omega} \\ &= -0.67 \text{ A} \end{aligned}$$

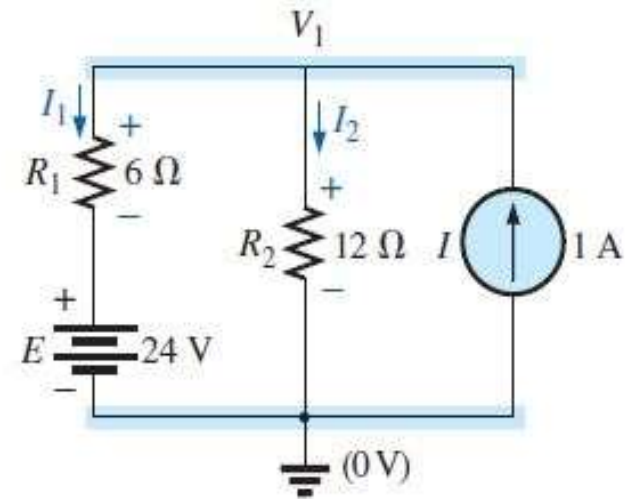

**FIG. 8.48**


*Applying Kirchhoff's current law to the node  $V_1$ .*



# NODAL ANALYSIS

The minus sign indicates that the current  $I_1$  has a direction opposite to that appearing in Fig. 8.48.

$$I_2 = \frac{V_1}{R_2} = \frac{20 \text{ V}}{12 \Omega} = 1.67 \text{ A}$$

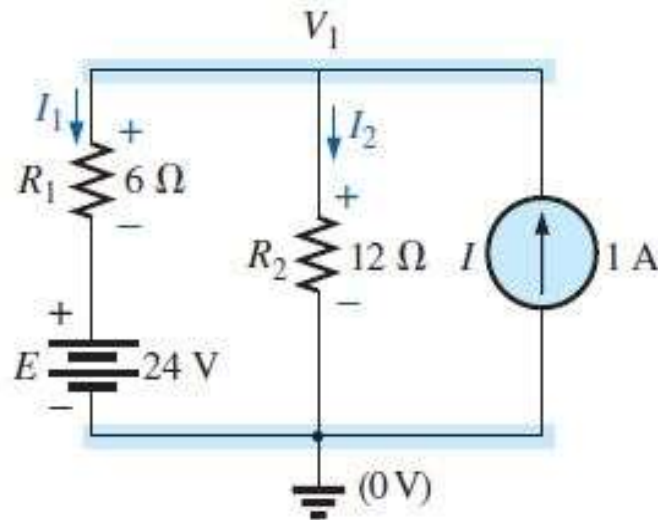


**FIG. 8.48**

*Applying Kirchhoff's current law to the node  $V_1$ .*

# NODAL ANALYSIS

**EXAMPLE 8.20** Apply nodal analysis to the network in Fig. 8.49

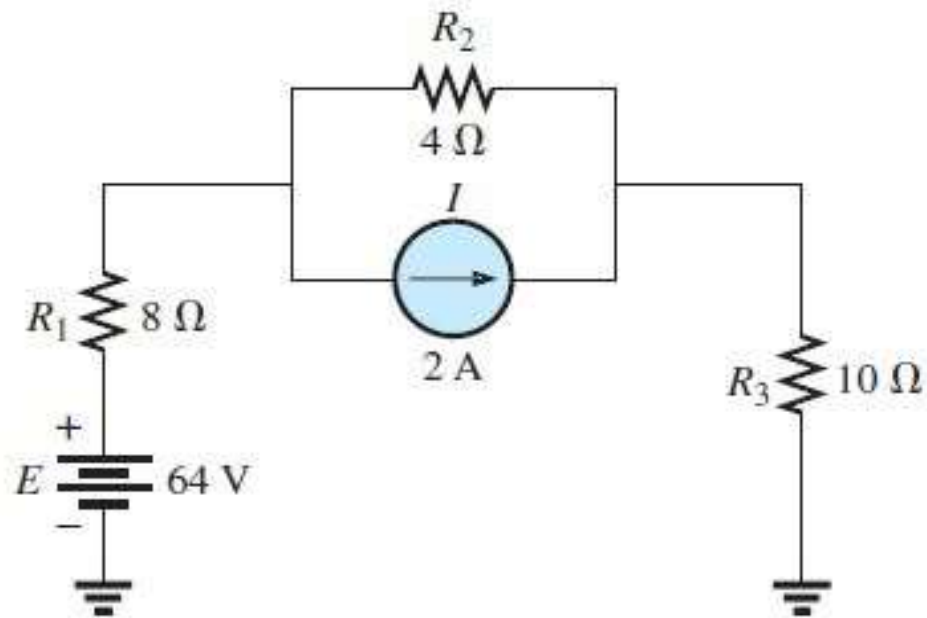


**FIG. 8.49**  
*Example 8.20.*

# NODAL ANALYSIS

## ***Solution:***

*Steps 1 and 2:* The network has three nodes, as defined in Fig. 8.50, with the bottom node again defined as the reference node (at ground potential, or zero volts), and the other nodes as  $V_1$  and  $V_2$

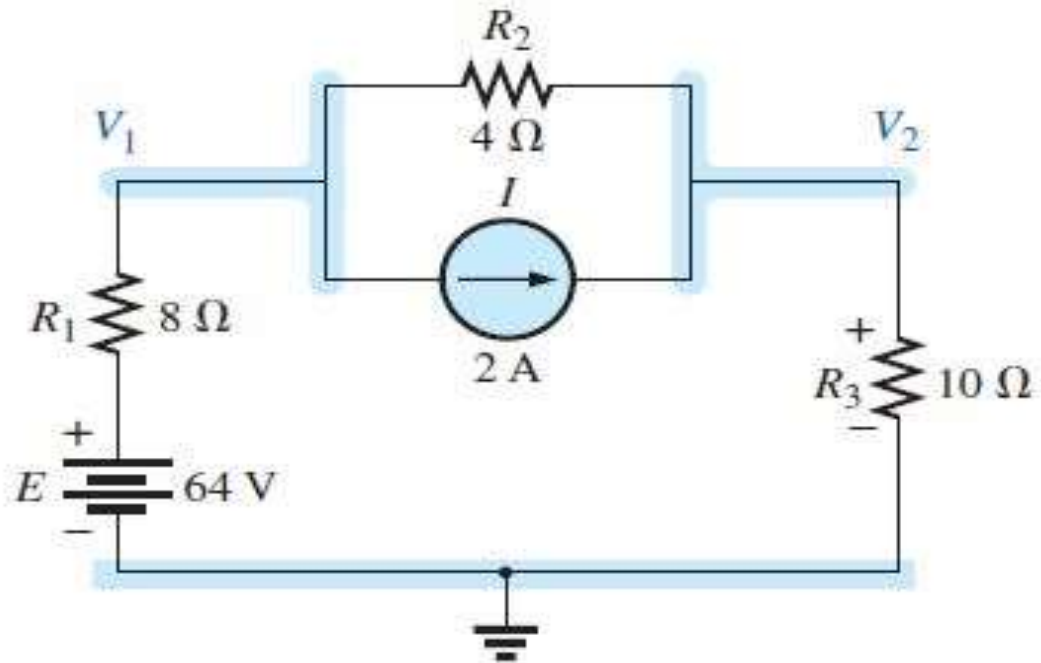


**FIG. 8.50**

*Defining the nodes for the network in Fig. 8.49.*

# NODAL ANALYSIS

## ***Solution:***

*Step 3:* For node  $V_1$ , the currents are defined as shown in Fig. 8.51 and Kirchhoff's current law is applied:

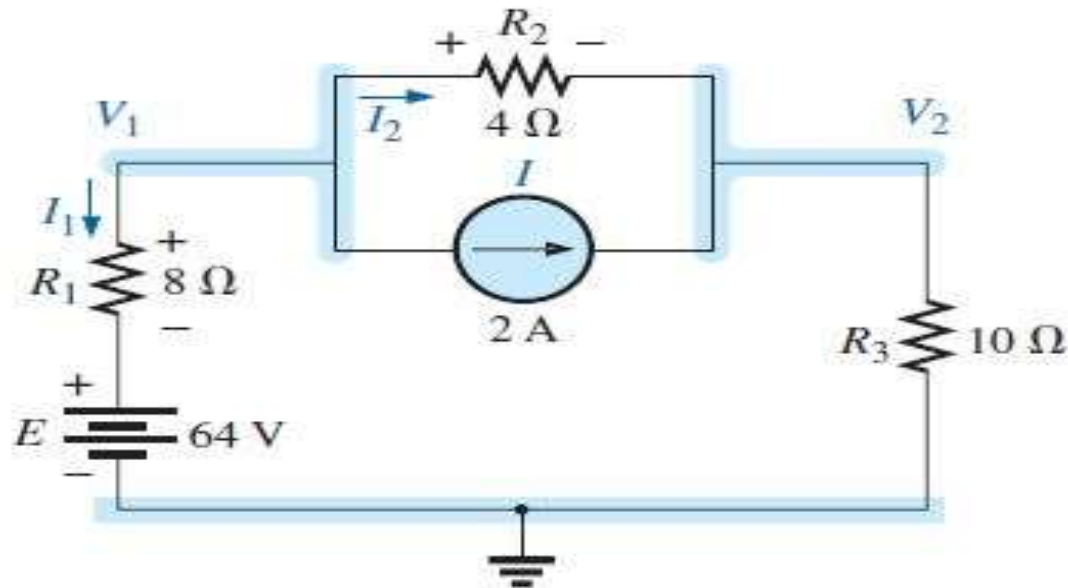

**FIG. 8.51**  
*Applying Kirchhoff's current law to node  $V_1$ .*

# NODAL ANALYSIS

$$0 = I_1 + I_2 + I$$

with

$$I_1 = \frac{V_1 - E}{R_1}$$

and

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{V_1 - V_2}{R_2}$$

so that

$$\frac{V_1 - E}{R_1} + \frac{V_1 - V_2}{R_2} + I = 0$$

or

$$\frac{V_1}{R_1} - \frac{E}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} + I = 0$$

and

$$V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left( \frac{1}{R_2} \right) = -I + \frac{E}{R_1}$$

Substituting values:

$$V_1 \left( \frac{1}{8 \Omega} + \frac{1}{4 \Omega} \right) - V_2 \left( \frac{1}{4 \Omega} \right) = -2 \text{ A} + \frac{64 \text{ V}}{8 \Omega} = 6 \text{ A}$$

For node  $V_2$  the currents are defined as shown in Fig. 8.52, and Kirchhoff's current law is applied:

$$I = I_2 + I_3$$

with

$$I = \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3}$$

or


$$I = \frac{V_2}{R_2} - \frac{V_1}{R_2} + \frac{V_2}{R_3}$$

and

$$V_2 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) - V_1 \left( \frac{1}{R_2} \right) = I$$

Substituting values:

$$V_2 \left( \frac{1}{4 \Omega} + \frac{1}{10 \Omega} \right) - V_1 \left( \frac{1}{4 \Omega} \right) = 2 \text{ A}$$

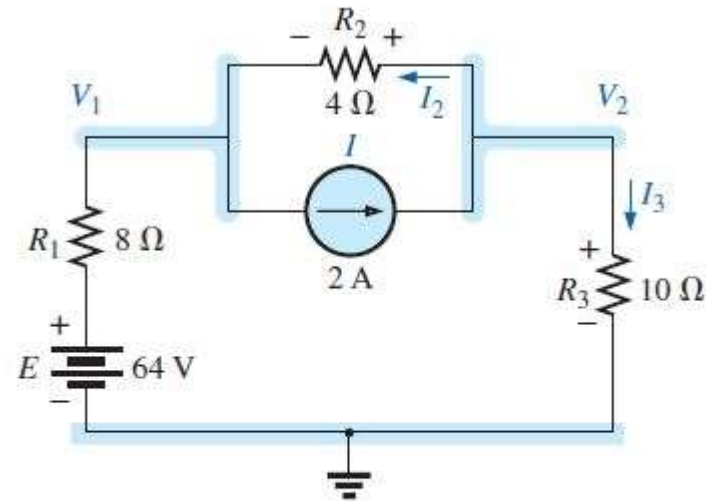

**FIG. 8.52**


*Applying Kirchhoff's current law to node  $V_2$ .*

# NODAL ANALYSIS

*Step 4:* The result is two equations and two unknowns:

$$\begin{aligned} V_1 \left( \frac{1}{8 \Omega} + \frac{1}{4 \Omega} \right) - V_2 \left( \frac{1}{4 \Omega} \right) &= 6 \text{ A} \\ -V_1 \left( \frac{1}{4 \Omega} \right) + V_2 \left( \frac{1}{4 \Omega} + \frac{1}{10 \Omega} \right) &= 2 \text{ A} \end{aligned}$$

---

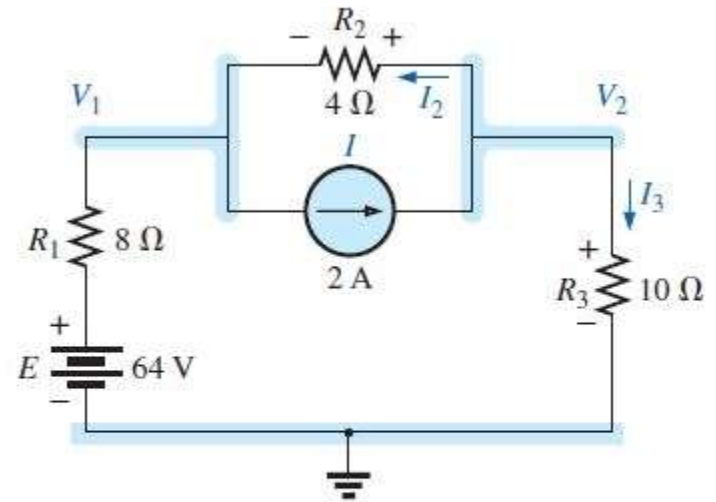

**FIG. 8.52**

*Applying Kirchhoff's current law to node  $V_2$ .*

# NODAL ANALYSIS

which become

$$\begin{aligned} 0.375V_1 - 0.25V_2 &= 6 \\ -0.25V_1 + 0.35V_2 &= 2 \end{aligned}$$

Using determinants,

$$\begin{aligned} V_1 &= 37.82 \text{ V} \\ V_2 &= 32.73 \text{ V} \end{aligned}$$

Since  $E$  is greater than  $V_1$ , the current  $I_1$  flows from ground to  $V_1$  and is equal to


$$I_{R_1} = \frac{E - V_1}{R_1} = \frac{64 \text{ V} - 37.82 \text{ V}}{8 \Omega} = 3.27 \text{ A}$$

The positive value for  $V_2$  results in a current  $I_{R_3}$  from node  $V_2$  to ground equal to

$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{V_2}{R_3} = \frac{32.73 \text{ V}}{10 \Omega} = 3.27 \text{ A}$$

Since  $V_1$  is greater than  $V_2$ , the current  $I_{R_2}$  flows from  $V_1$  to  $V_2$  and is equal to

$$I_{R_2} = \frac{V_1 - V_2}{R_2} = \frac{37.82 \text{ V} - 32.73 \text{ V}}{4 \Omega} = 1.27 \text{ A}$$

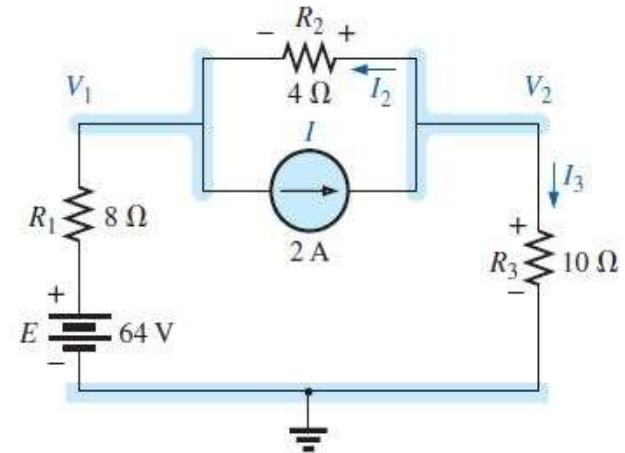

**FIG. 8.52**

*Applying Kirchhoff's current law to node  $V_2$ .*